



Physics Worksheet

Electric Circuits

Name: _____ Student #: _____ Student Email #: _____

1. The following question concerns RLC circuits

(a) Search online and draw a diagram of an RLC circuit and indicate all the components

(b) Look up what the "equation of motion" of an RLC circuit is. What motion does this equation describe?

(c) What are RLC circuits used for?

2. What is the effective resistance of the below delta formation resistor if $R_1 = 1\Omega$, $R_2 = 4\Omega$, and $R_3 = 5\Omega$. (Hint: look up "Delta-Wye Circuit Transformations")

